4 Way Switch (Power and Light to the Same Switch) (Schematic)
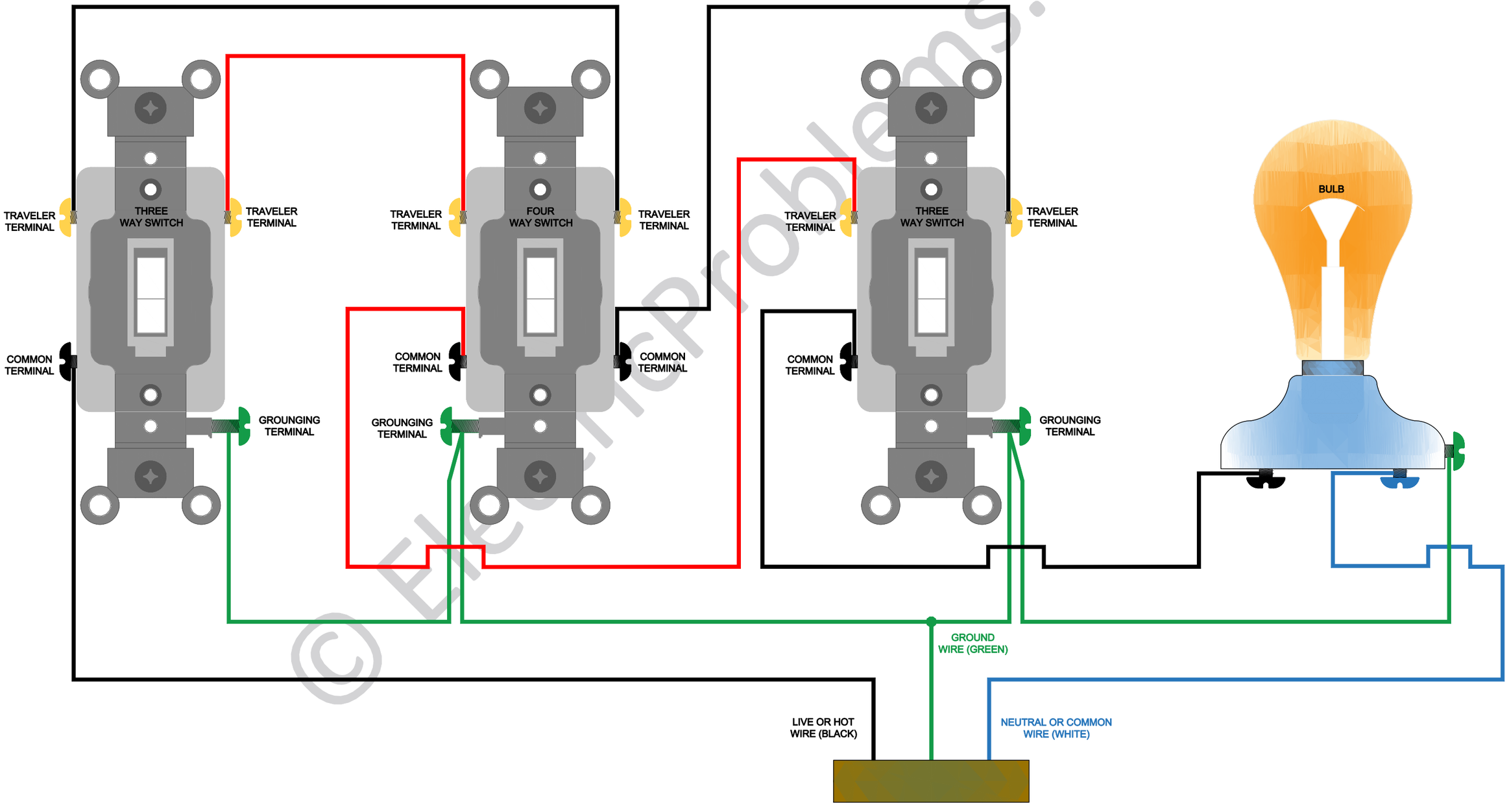
© ElectricProblems.com